

Gustav KIRCHHOFF'S LAWS → 1845 → German Scientist


(i) Kirchhoff's Voltage Law (KVL)

(ii) Kirchhoff's Current Law (KCL)

KVL → The sum of all voltages around a loop is equal to zero.

Mathematically:-

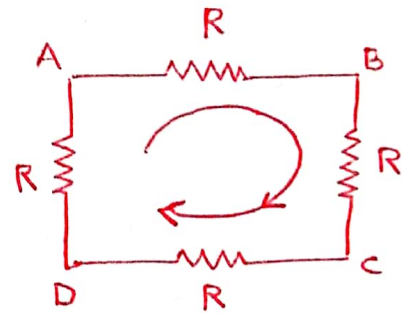
$$V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$



[Note: $V = IR$]

Method-1

Example: 1

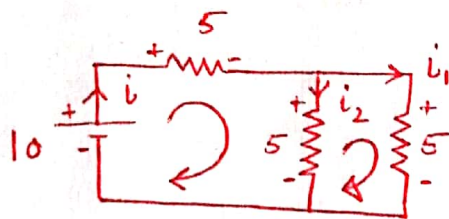

$$\begin{aligned} 10 - 5i - 5i_2 &= 0 & 5i_2 - 5i_1 &= 0 \\ 5i + 5i_2 &= 10 & i_1 &= i_2 \end{aligned} \quad \text{--- (1) \quad (2)}$$

$$\begin{aligned} i_1 + i_2 &= i & \text{--- (3)} \\ 2i_1 &= i \\ i_1 = i_2 &= i/2 & \text{--- (4)} \end{aligned}$$

From (1) and (4)

$$5 \times 2i_2 + 5i_2 = 10$$

$$15i_2 = 10$$

$$i_2 = \frac{10}{15} = \frac{2}{3} = i_1$$

from (3)


$$\frac{2}{3} + \frac{2}{3} = i \Rightarrow \frac{4}{3}$$

(ii) KCL states that, total current or charge entering a junction or Node is exactly equal to the charge leaving the node.

In other words the algebraic sum of all the currents entering and leaving a node must be equal to zero.

$$I_{\text{going}} + I_{\text{entering}} = 0$$


Conservation of Charge.

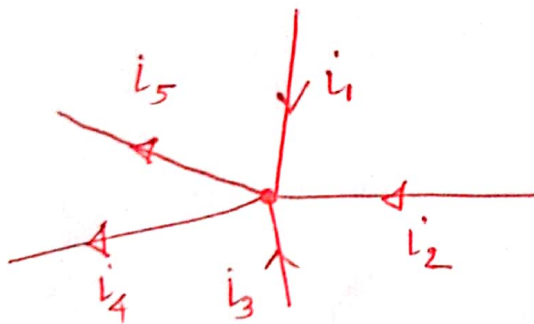

$$i_1 + i_2 + i_3 = i_4 + i_5 \quad (1)$$


$$i_1 + i_2 + i_3 - i_4 - i_5 = 0 \quad (2)$$

Voltage Divider Rule.

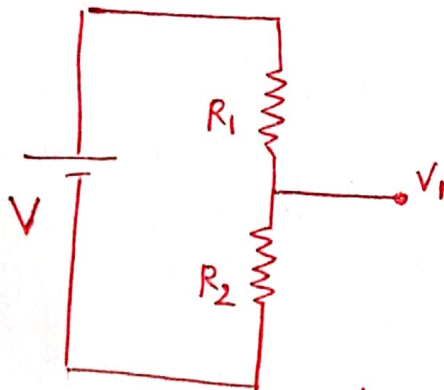


$$V_1 = \frac{V R_2}{R_1 + R_2}$$

Ex. 1

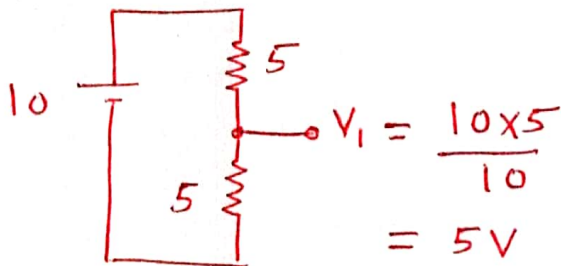

$$V_1 = \frac{10 \times 5}{10} = 5V$$

Example-1

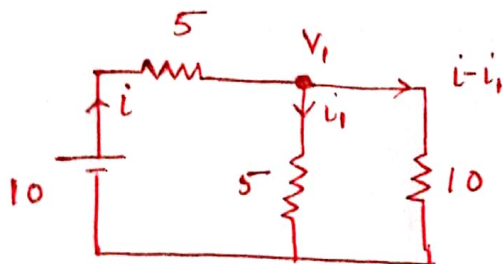


$$V_1 = \frac{10 \times 10 / \frac{3}{3}}{5 + 10 / \frac{3}{3}} = \frac{100 \times 3}{3[15+10]} = \frac{100}{25} = 4V$$

$$V_1 = i_1 \times 5 \Rightarrow i_1 = \frac{4}{5} = 0.8$$

$$i - i_1 = i_{10} = 0.4$$


Current Divider Rule.

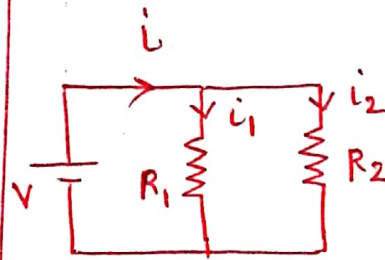

$$i_1 = \frac{R_2 I}{R_1 + R_2}$$

$$i_2 = \frac{I \times R_1}{R_1 + R_2}$$


Ex. 1

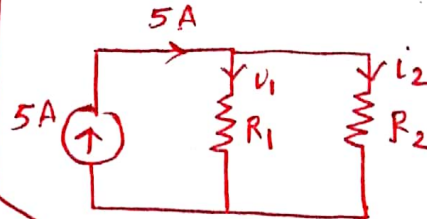

$$i_1 = \frac{5 \times R_2}{R_1 + R_2}$$

$$i_2 = \frac{5 \times R_1}{R_1 + R_2}$$

Example-1

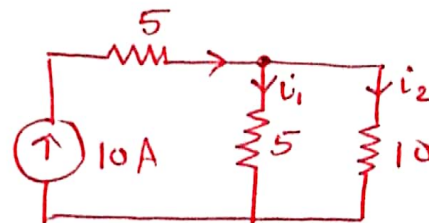

$$\text{KVL } \times \quad i_1 = \frac{10 \times 10}{25}$$

$$10 = i_1 + i_2 \quad i_2 = \frac{10 \times 5}{25}$$