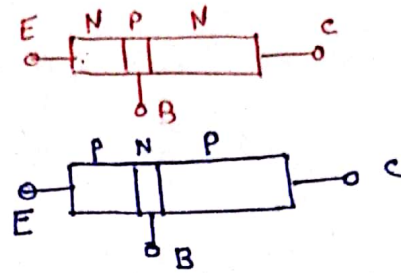


BJT - Bipolar Junction Transistor

Two type

npn

npn



Note:- Q.1 which one is better

NPN - Best
Both operation same.

Reason: (1) npn Fast
(2) small in size

Because: Mobility of e^- are greater as compared to hole mobility.

$\mu_n > \mu_p$
Mobility of e^- mobility of holes

Q.2 How many terminal and how many Junction?

Ans:- 3 terminal and Two Junction as seen from above fig

Q.3 How many configuration possible:


3 Configuration possible.

- ↳ Common Emitter
- ↳ Common Base
- ↳ Common Collector

Q.4 Which Configuration is best -

Common Emitter Configuration mostly Used.
Have high power gain and useful for amplification.

Q.5

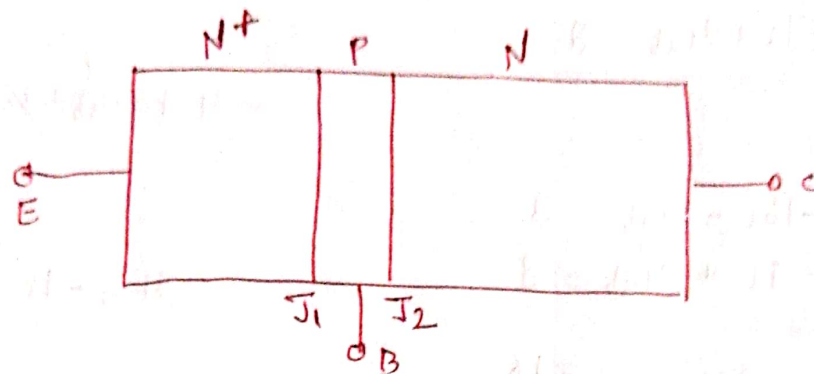

Size: $C > E > B$.

Doping: $E > C > B$

Q.6

Symmetric device or Asymmetric

↓ BJT is asymmetric device


as they have different size and doping profile ← We cannot interchange Emitter, Base, Collector

Q.7 We can apply external voltage to bias J_1 and J_2 Junction. → Base on J_1 and J_2 Junction biasing we can make our BJT to operate in Four Modes

	J_1	J_2	
I - Mode	FB	RB	→ Active Mode → used for amplify
II - Mode	FB	FB	→ Saturation Mode
III - Mode	RB	RB	→ Cutoff mode
IV - Mode	RB	FB	→ Reverse active → No such useful application

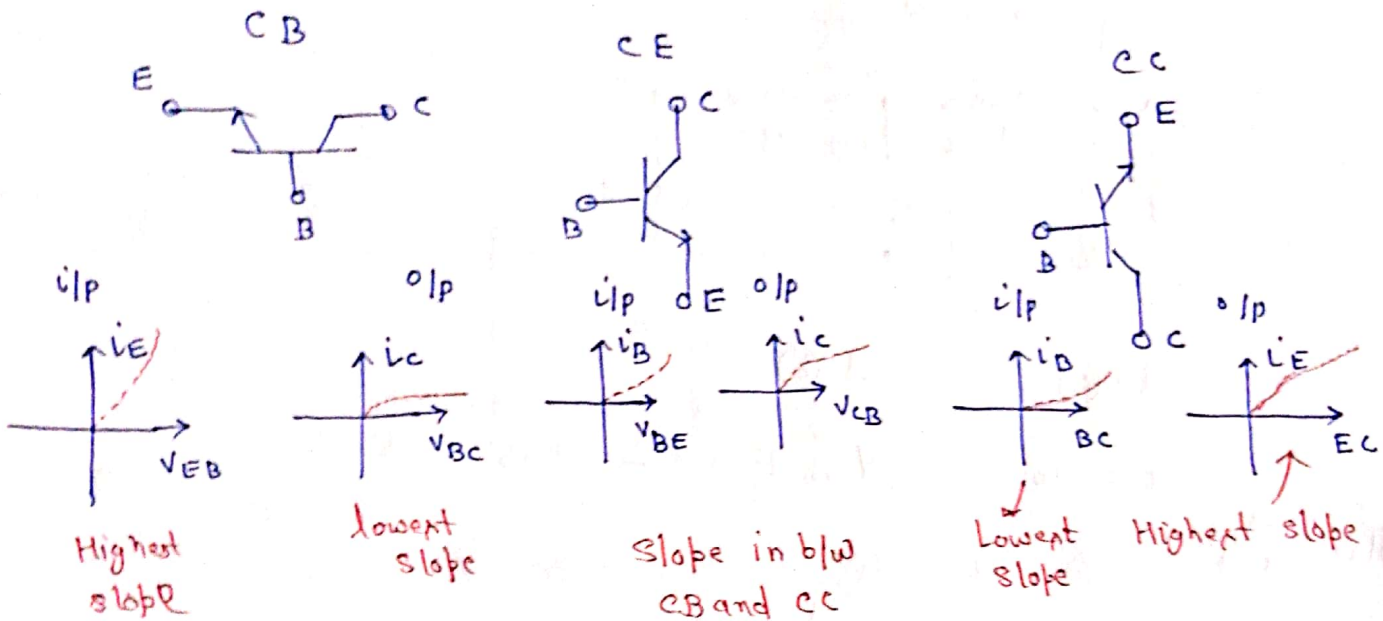Q.8

Characteristic $\begin{cases} \text{i/p} \rightarrow \text{input} \\ \text{o/p} \rightarrow \text{output} \end{cases}$



Current Gain (α)

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E$$

$$\alpha < 1$$

First of all we will draw characteristic of this

Current gain (β)

$$\beta = \frac{I_C}{I_B} \Rightarrow I_C = \beta I_B$$

$$\therefore I_E > I_C > I_B$$

$$\beta > 1$$

Current gain (γ)

$$\gamma = \frac{I_E}{I_B}$$

$$I_E = \gamma I_B$$

$$\gamma \gg 1$$


Q.9

Operation of BJT in Active Mode and with. CE Configuration.

\rightarrow Very important Mostly Used.

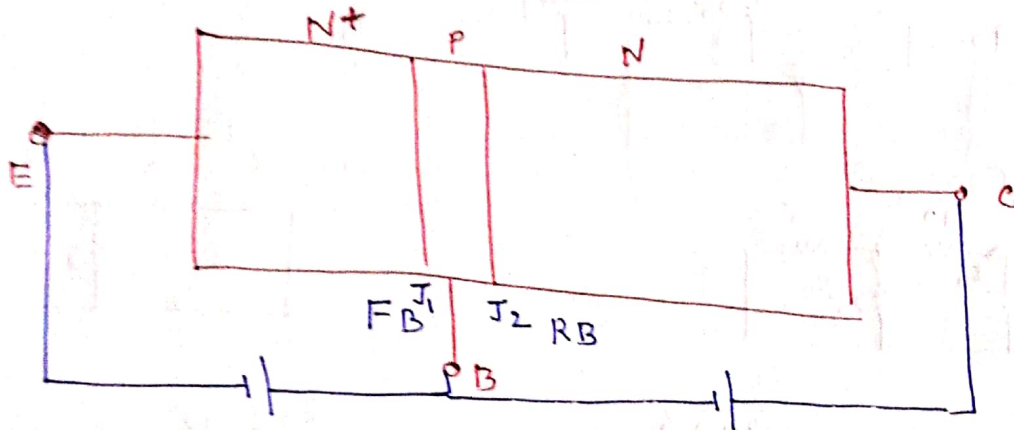
Q.10

BJT \rightarrow Common base \rightarrow Active mode is drawn below



\Rightarrow $\left. \begin{matrix} J_1 \\ J_2 \end{matrix} \right\} \begin{matrix} \text{FB} \\ \text{RB} \end{matrix}$ First elementary Condition so that how our BJT work in Active mode.

Q.11

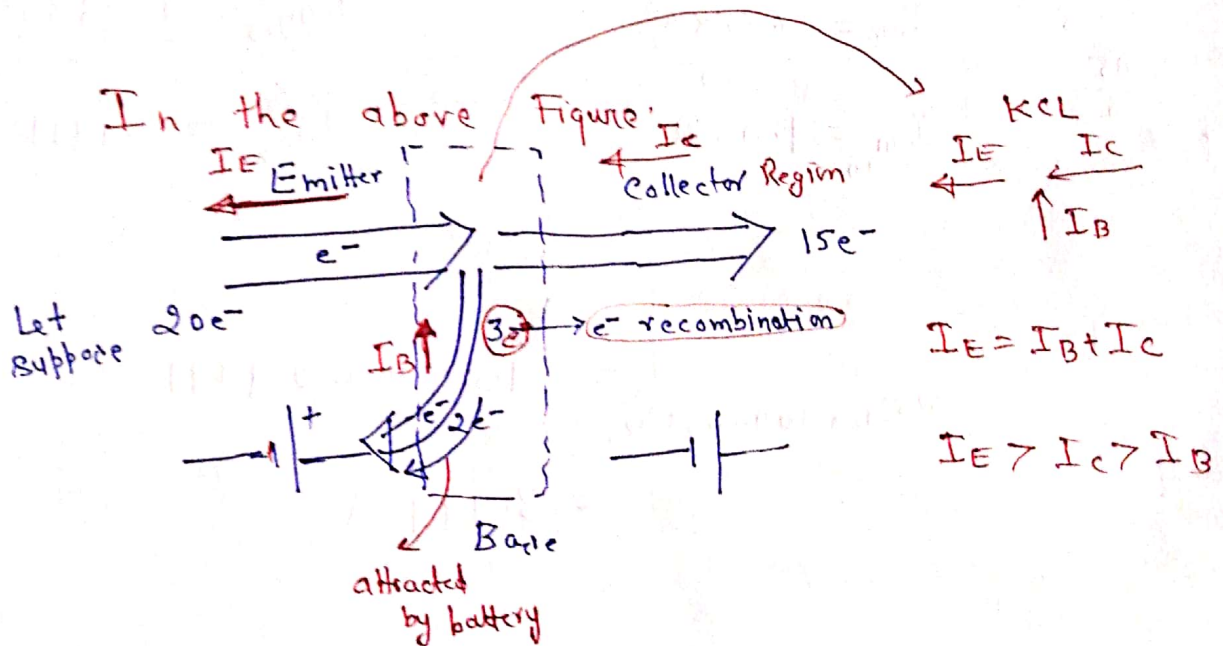

Q.12

GAIN occurs in BASE REGION