

Name = Navej Singh

Course = B-TECH comp sci

Sub code = BEE DIT1003

adm. no = 21SCSE1011675

Date = 17/1/2022

Sec = 24/P2 batch

① MMF = Magneto Motive force (force that tends to establish the flux through magnetic circuit).

Reluctance = Reluctance oppose the production of magnetic flux in magnetic circuit

$$\text{Reluctance} = \frac{\text{mmf}}{\text{flux}}$$

②  $i = 50 \sin 314t$

$$i = i_0 \sin \omega t$$

③ maximum current ( $i_0$ ) = 50 A

④

$$\omega = \frac{2\pi}{T} = 2\pi$$

$$T = \frac{2\pi}{\omega} = \frac{2 \times 3.14}{314 \times 100} = 0.02$$

Time period |  $T = 0.02 \text{ s}$




③ Expression for instantaneous voltage



$$V = V_m \sin \omega t$$

Expression for instantaneous current

$$i = i_m \sin \omega t$$

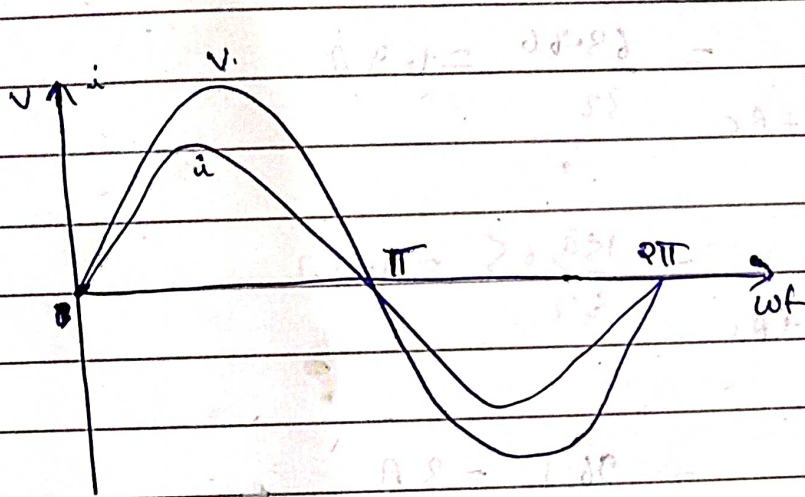

Wave form

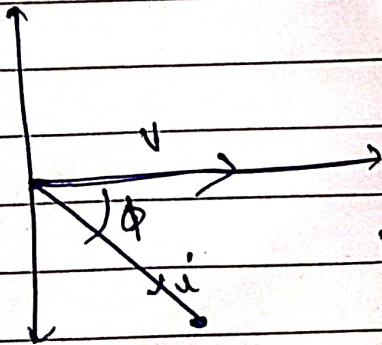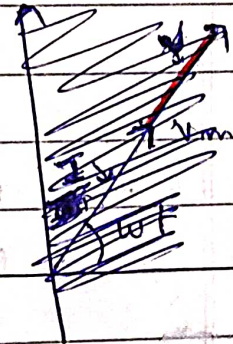

Phasor diagrams

⑥

Power,  $P = vi$

$$P = (V_m \sin \omega t) (i_m \sin \omega t)$$

$$P = \frac{V_m i_m}{2} \sin^2 \omega t = \frac{V_0}{\sqrt{2}} \cdot \frac{i_0}{\sqrt{2}} (1 - \cos 2\omega t)$$

$$P = \frac{V_0}{\sqrt{2}} \cdot \frac{i_0}{\sqrt{2}} - \frac{V_0}{\sqrt{2}} \cdot \frac{i_0}{\sqrt{2}} \cos 2\omega t$$




Neeraj Singh

Date = 18/11/2022

Page No.

(4)

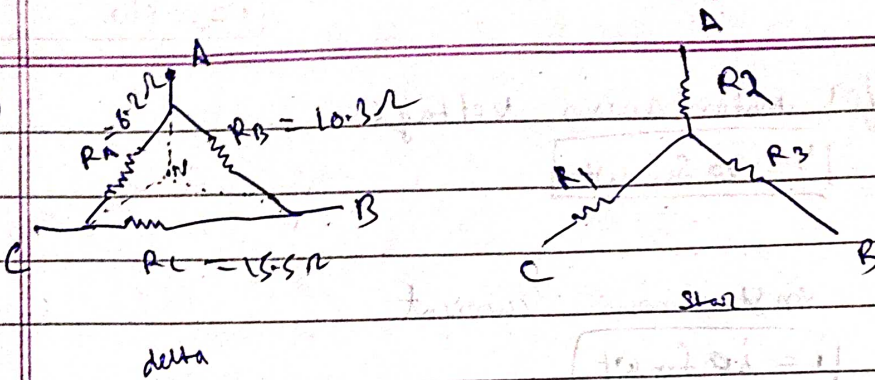

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{63.86}{32} = 1.9 \Omega$$


$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{159.65}{32} = 4.9 \Omega$$

$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{96.1}{32} = 3 \Omega$$

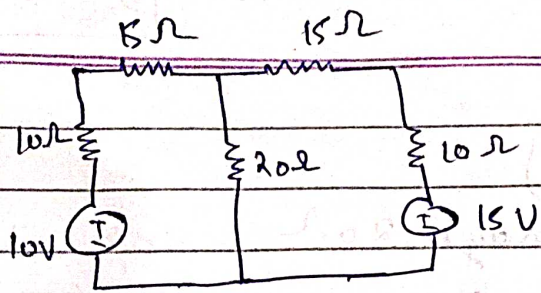(5)

ac<sup>m</sup> to Super position theorem, in any linear, bilateral multi source network, the current or voltage across any branch can be calculated by taking one source at a time and replacing the other active source by their internal resistance.






across 20 ohm

There are 2 active sources.

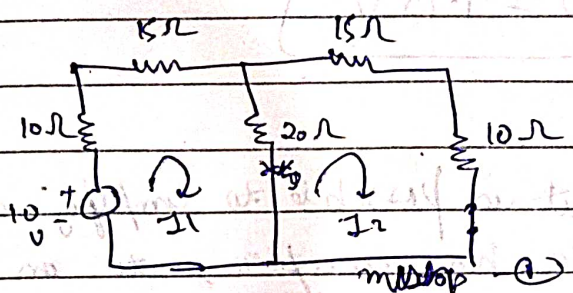taking 10V and replacing all other sources by their int. resis.



①

$$-45I_1 + 20I_2 = -10$$

$$-9I_1 + 4I_2 = -2$$

$$9I_1 - 4I_2 = 2 \quad \text{--- (1)}$$

keep 2 mesh - 2

$$-45I_2 + 20I_1 = 0$$

$$45I_2 = 20I_1$$

$$9I_2 = 4I_1 \quad \text{--- (2)}$$

Solving (1) and (2)

$$I_1 = 0.18 \text{ A}$$

$$I_2 = 0.082 \text{ A}$$


Current through 20 ohm

$$I' = I_1 - I_2$$

$$I' = 0.098 \text{ A} \quad \text{indirect of } I_1, I_2$$

②

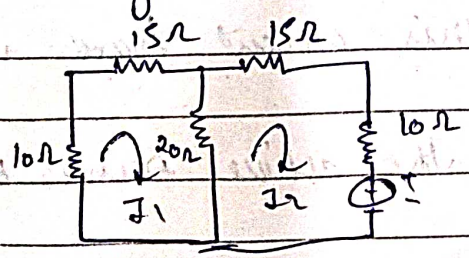Taking 15V source and removing all other sources by their int. R.



mesh - 1

$$-45I_1 + 20I_2 = 0 \quad \text{--- (1)}$$

mesh - (2)

$$-45I_2 + 20I_1 = 10 \quad \text{--- (2)}$$

Solving (1) and (2)

$$I_2 = -1.38 \text{ A}$$

$$I_1 = 0.61 \text{ A}$$

$$\text{Current through } 20\Omega = I_1 - I_2 = 0.61 - 1.38 = -0.77 \text{ A}$$

$$I' = -0.77 \text{ A}$$



$$I = I' + I''$$

$$I = 0.099 + (-0.77A)$$

$$I = -0.672A \text{ through } 20\Omega$$

$$\text{Voltage across } 20\Omega = V = iR$$

$$= V = 0.67 \times 20$$

$$V = 1.19V$$

- ⑥ Norton theorem states that it is possible to simplify any linear circuit, no matter how complex, to an equivalent circuit with just a single current source and parallel connected to a load. Just as with Thevenin's Theorem, the qualification of linear is identical to that found in the Superposition theorem: all underlying equations must be linear.

### ⑦ Steps

- ① Identify load resistor  $R_L$
- ② Replace  $R_L$  with short circuit branch
- ③ The current flowing through this circuit branch will be the Norton current  $I_N$
- ④ Remove  $R_L$  and replace all the active sources by their internal resistance.
- ⑤ The equivalent resistance across the two open ends will be the Norton resistance  $R_N$
- ⑥ Draw Norton's eq<sup>n</sup> circuit
- ⑦ Calculate  $I_L$  using the id only

$$I_L = \frac{I_N R_N}{R_N + R_L}$$



Neeraj Singh

Sem-24, P2

adm - 213CSGL04675

Date: 08/1/22

Page No.

### Comparison

- Norton theorem uses a current source, whereas Thevenin's theorem uses a voltage source
- Thevenin theorem uses a resistor in series, while Norton uses a resistor set in parallel with the source