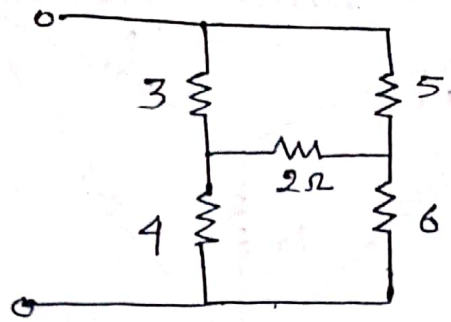



CONCEPT:-
Exo 5




① Balanced condition
 $\frac{5}{3} = 1.6$ also fails.
 $\frac{6}{4} = 1.5$

② Neither || nor series connection is seen.

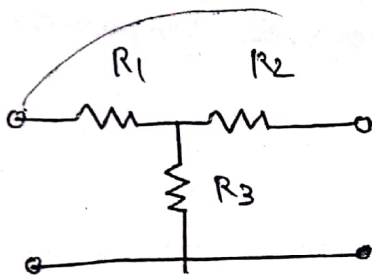
Note - When element are connected neither in series nor in parallel to reduce the n/w. STAR-DELTA Transformation is used.




T

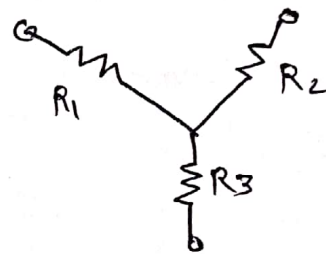

Y or Delta-Star

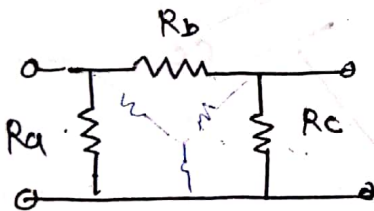

π

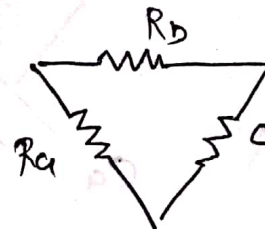

Delta.

Delta to Star:-

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

Star to Delta


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$
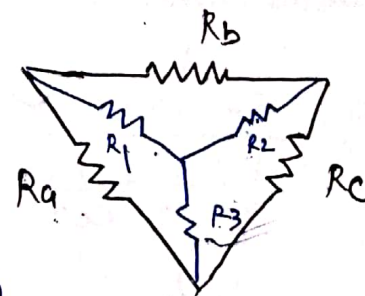
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$




②

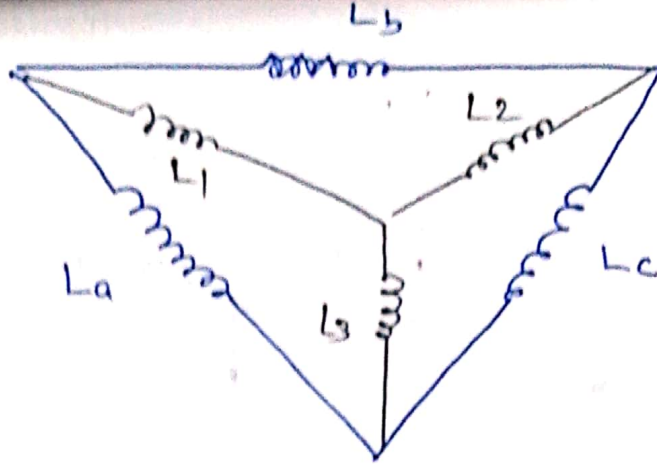

Note:- The procedure of transformation from star to delta and delta to star. for the resistor, inductor, & impedance is same.

③

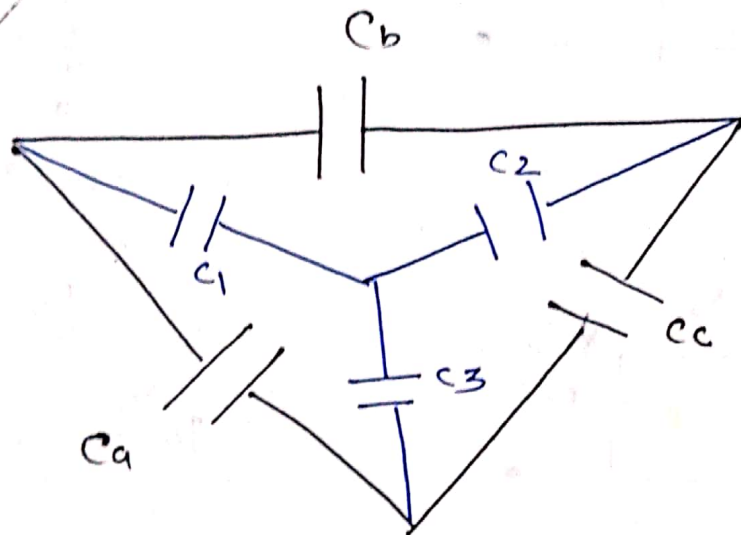

Delta to star:-

$$\frac{1}{C_1} = \frac{\frac{1}{C_a} \frac{1}{C_b}}{\frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}}$$

$$\frac{1}{C_2} = \frac{\frac{1}{C_b} \frac{1}{C_c}}{\frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}}$$

$$\frac{1}{C_3} = \frac{\frac{1}{C_a} \frac{1}{C_c}}{\frac{1}{C_a} + \frac{1}{C_b} + \frac{1}{C_c}}$$

star to delta:-


$$C_a = \frac{\frac{1}{C_1} \frac{1}{C_2} + \frac{1}{C_2 C_3} + \frac{1}{C_3 C_1}}{\frac{1}{C_2}}$$

$$C_b = \frac{1}{\frac{1}{C_3}}$$

$$C_c = \frac{1}{\frac{1}{C_1}}$$

Prob: ①




⇒ Find Req. b/w A & B

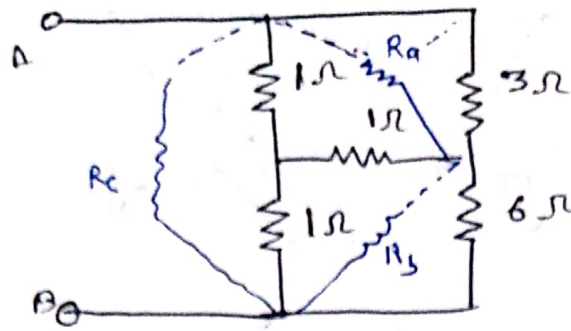

$$R_a = \frac{3}{1} = 3\Omega$$

$$R_b = 3\Omega$$

$$R_c = 3\Omega$$

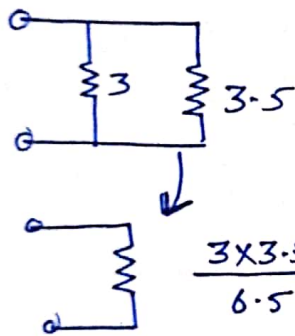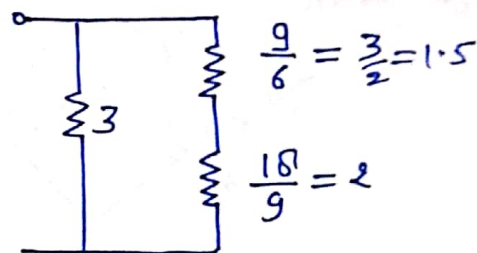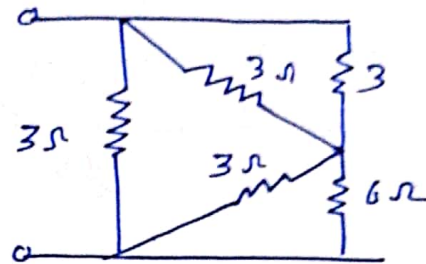

$$\frac{3 \times 3.5}{6.5} = \frac{3 \times 35}{65} = \frac{7 \times 3}{13} = \frac{21}{13} = 1.59\Omega$$

$$\begin{array}{r} 13 \\ \times 6 \\ \hline 90 \end{array} \quad \begin{array}{r} 13 \\ \times 5 \\ \hline 65 \end{array} \quad \begin{array}{r} 150 \\ \times 4 \\ \hline 120 \end{array}$$

Note: -

① When resistor of equal value transformed $(Y \leftrightarrow \Delta)$ from star to delta resistance \uparrow by 3 times.

② When capacitor of equal value transformed from star to Delta capacitance decreases by 3 times.