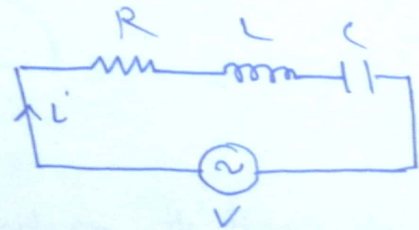


RESONANCE

① For occurrence of resonance in any ckt, the ckt should consist of two energy storing element



② The ckt is said to be in resonance when current is in phase with source voltage.

③ The frequency at which $X_L = X_C$ is called as resonant frequency.



④ Resonant frequency indicates the rate at which energy transformation is done b/w inductor and Capacitor.

$$\frac{V_L = V_C}{I X_L = I X_C}$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

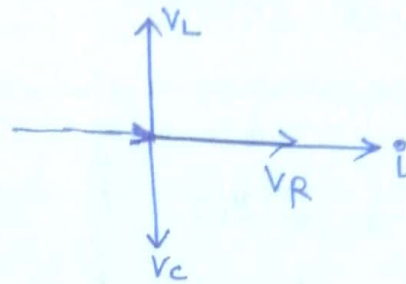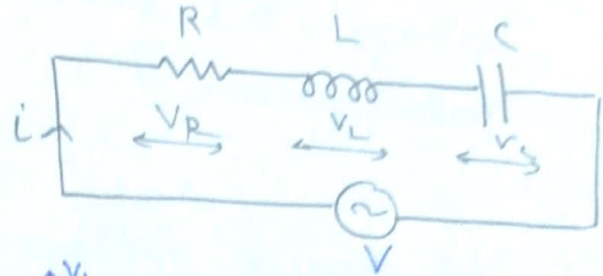

$$\therefore V_R = V$$

At Resonance:-

$$① \quad Z = R + j(X_L - X_C)$$

$$Z_{\min} = R \quad \because X_L = X_C$$

$$② \quad \underline{I_{\max}} = \frac{V}{Z_{\min}} = \frac{V}{R}$$

$$③ \quad \underline{\cos \theta = 1} \quad \left[\text{As } V \text{ and } i \text{ are in phase, } \theta = 0 \right]$$

power factor = 1

$$④ \quad \underline{V_R = V} \quad \begin{array}{l} V_R \rightarrow \text{active component} \\ V_L \text{ and } V_C \rightarrow \text{Reactive component} \end{array}$$

$$⑤ \quad \underline{\text{Net reactive Voltage} = 0}$$

Voltage Magnification:-

Voltage across inductor and voltage across capacitor is greater than source voltage. This phenomenon is called as voltage magnification.

Variation of voltage across inductor and capacitor w.r.t frequency:-

$$V_c = I X_c$$

$$X_c = \frac{1}{2\pi f C}$$

$$X_L = 2\pi f L$$

$$f = 0 \quad X_c = \infty \quad X_L = 0$$


$$V_c = V$$

$$f \uparrow \quad X_c \downarrow \quad X_L \uparrow \quad Z \uparrow \quad I \downarrow$$
$$V_c \downarrow$$

$$f \uparrow \quad X_c \downarrow \quad X_L \uparrow$$
$$\infty \quad 2$$

$$|X| = |X_L - X_c| \quad \downarrow \downarrow$$
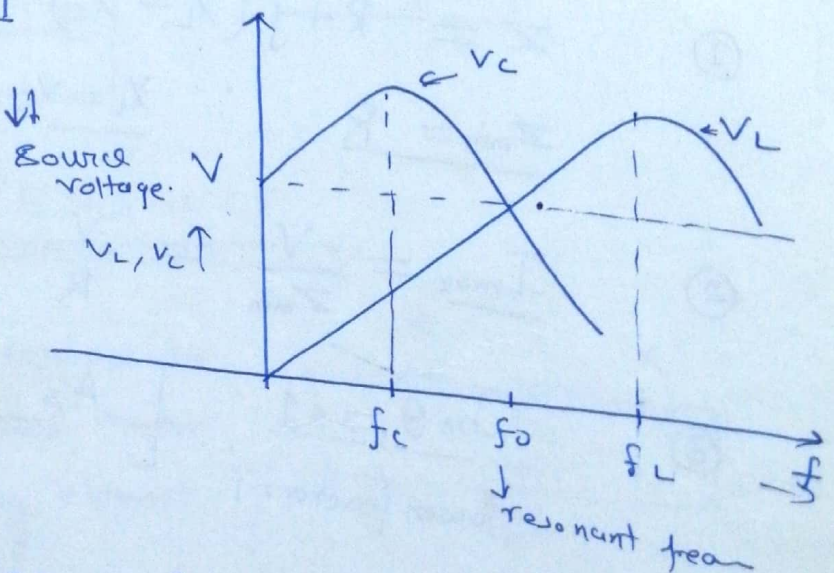
$$Z \downarrow \quad I = \frac{V}{Z} \quad I \uparrow \uparrow \quad V_c \uparrow$$



$$V_c = I X_c$$

$$V_c = \frac{V}{\sqrt{R^2 + (X_L - X_c)^2}} X_c$$

$$V_c = \frac{V(\frac{1}{\omega c})}{\sqrt{R^2 + (\omega L - \frac{1}{\omega c})^2}} \quad \text{--- (1)}$$

differentiating w.r.t ω 2-time and equating to 0 we get

$$f_c = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \left(\frac{R^2 C}{2L}\right)}$$

Case II

$$V_L = I X_L$$

$$X_L = 2\pi f L$$

$$f=0 \quad X_c = \infty \quad X_L = 0 \quad Z = \infty$$

$$I = 0$$

$$V_L = 0$$

$$f \uparrow$$

$$X_c \downarrow$$

$$X_L \uparrow$$

$$|X| = (X_L - X_c) \downarrow \downarrow \quad Z \uparrow \uparrow$$

$$I \uparrow \uparrow = \frac{V}{Z \downarrow \downarrow}$$

When

$$f \uparrow \uparrow$$

$$X_L \uparrow \uparrow$$

$$X_c \downarrow \downarrow$$

$$Z = R + j(X_L - X_c) \uparrow \uparrow$$

$$I \downarrow \downarrow \downarrow$$

$$V_L = I X_L$$

$$V_L = \frac{V(\omega L)}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$f_L = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{1}{1 - \left(\frac{R^2 C}{2L}\right)}} \quad \approx \frac{\omega}{2}$$

Quality factor (Q-factor)



$$Q = \frac{V_L(\text{or}) V_C}{V}$$

$$Q = \frac{V_L}{V} = \frac{V_L}{V_R} = \frac{\text{Reactive component of voltage}}{\text{Active component of voltage.}}$$

$$Q = \frac{V_L}{V_R} = \frac{I X_L}{I R} = \frac{\omega L}{R} = \frac{\omega L}{R}$$

$$\text{But } \omega = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{Q_L}{P} = \frac{I^2 X_L}{I^2 R} = \frac{X_L}{R} \quad \left[\begin{array}{l} Q_L \Rightarrow \text{Reactive inductive power} \\ P = \text{active power.} \end{array} \right]$$

$$Q = \frac{V_c}{V} = \frac{X_c}{R} = \frac{1}{\omega RC}$$

$$Q = 2\pi \frac{\text{max. energy stored in the elct}}{\text{power dissipation per cycle.}}$$